

## 7-1 THE JFET

The JFET (junction field-effect transistor) is a type of FET that operates with a reverse-biased  $pn$  junction to control current in a channel. Depending on their structure, JFETs fall into either of two categories,  $n$  channel or  $p$  channel.


After completing this section, you should be able to

- Explain the operation of JFETs
- Identify the three terminals of a JFET
- Explain what a channel is
- Describe the structural difference between an  $n$ -channel JFET and a  $p$ -channel JFET
- Discuss how voltage controls the current in a JFET
- Identify the symbols for  $n$ -channel and  $p$ -channel JFETs

Figure 7-1(a) shows the basic structure of an  $n$ -channel JFET (junction field-effect transistor). Wire leads are connected to each end of the  $n$ -channel; the **drain** is at the upper end, and the **source** is at the lower end. Two  $p$ -type regions are diffused in the  $n$ -type material to form a **channel**, and both  $p$ -type regions are connected to the **gate** lead. For simplicity, the gate lead is shown connected to only one of the  $p$  regions. A  $p$ -channel JFET is shown in Figure 7-1(b).

FIGURE 7-1

 A representation of the basic structure of the two types of JFET.



## Basic Operation

To illustrate the operation of a JFET, Figure 7-2 shows dc bias voltages applied to an  $n$ -channel device.  $V_{DD}$  provides a drain-to-source voltage and supplies current from drain to source.  $V_{GG}$  sets the reverse-bias voltage between the gate and the source, as shown.

The JFET is always operated with the gate-source  $pn$  junction reverse-biased. Reverse biasing of the gate-source junction with a negative gate voltage produces a depletion region along the  $pn$  junction, which extends into the  $n$  channel and thus increases its resistance by restricting the channel width.

The channel width and thus the channel resistance can be controlled by varying the gate voltage, thereby controlling the amount of drain current,  $I_D$ . Figure 7-3 illustrates this concept. The white areas represent the depletion region created by the reverse bias. It is wider toward the drain end of the channel because the reverse-bias voltage between the gate and the drain is greater than that between the gate and the source. We will discuss JFET characteristic curves and some important parameters in Section 7-2.



 



FIGURE 7-2  
A biased *n*-channel JFET.

 

(a) JFET biased for conduction

 

 (b) Greater  $V_{GG}$  narrows the channel (between the white areas) which increases the resistance of the channel and decreases  $I_D$ .




(c) Less  $V_{GG}$  widens the channel (between the white areas) which decreases the resistance of the channel and increases  $I_D$ .

FIGURE 7-3  
Effects of  $V_{GS}$  on channel width, resistance, and drain current ( $V_{GG} = V_{GS}$ ).

## JFET Symbols

The schematic symbols for both  $n$ -channel and  $p$ -channel JFETs are shown in Figure 7-4. Notice that the arrow on the gate points “in” for  $n$  channel and “out” for  $p$  channel.

FIGURE 7-4  
JFET schematic symbols.

 

### SECTION 7-1 REVIEW

Answers are at the end of the chapter.

1. Name the three terminals of a JFET.
2. Does an  $n$ -channel JFET require a positive or negative value for  $V_{GS}$ ?
3. How is the drain current controlled in a JFET?

## 7-2 JFET CHARACTERISTICS AND PARAMETERS

In this section, you will see how the JFET operates as a voltage-controlled, constant-current device. You will also learn about cutoff and pinch-off as well as JFET transfer characteristics.

After completing this section, you should be able to

- Define, discuss, and apply important JFET parameters
- Explain ohmic area, constant-current area, and breakdown
- Define *pinch-off voltage*
- Describe how gate-to-source voltage controls the drain current
- Define *cutoff voltage*
- Compare pinch-off and cutoff
- Analyze a JFET transfer characteristic curve
- Use the equation for the transfer characteristic to calculate  $I_D$
- Use a JFET data sheet
- Define *transconductance*
- Explain and determine input resistance and capacitance
- Determine drain-to-source resistance

Consider the case when the gate-to-source voltage is zero ( $V_{GS} = 0$  V). This is produced by shorting the gate to the source, as in Figure 7-5(a) where both are grounded. As  $V_{DD}$  (and thus  $V_{DS}$ ) is increased from 0 V,  $I_D$  will increase proportionally, as shown in the graph of Figure 7-5(b) between points A and B. In this area, the channel resistance is essentially constant because the depletion region is not large enough to have significant effect. This is called the ohmic area because  $V_{DS}$  and  $I_D$  are related by Ohm's law.

 


FIGURE 7-5 The drain characteristic curve of a JFET for  $V_{GS} = 0$  showing pinch-off.

At point *B* in Figure 7-5(b), the curve levels off and  $I_D$  becomes essentially constant. As  $V_{DS}$  increases from point *B* to point *C*, the reverse-bias voltage from gate to drain ( $V_{GD}$ ) produces a depletion region large enough to offset the increase in  $V_{DS}$ , thus keeping  $I_D$  relatively constant.

**Pinch-Off Voltage**

For  $V_{GS} = 0$  V, the value of  $V_{DS}$  at which  $I_D$  becomes essentially constant (point *B* on the curve in Figure 7-5(b)) is the **pinch-off voltage**,  $V_p$ . For a given JFET,  $V_p$  has a fixed value. As you can see, a continued increase in  $V_{DS}$  above the pinch-off voltage produces an almost constant drain current. This value of drain current is  $I_{DSS}$  (Drain to Source current with gate Shorted) and is always specified on JFET data sheets.  $I_{DSS}$  is the *maximum* drain current that a specific JFET can produce regardless of the external circuit, and it is always specified for the condition,  $V_{GS} = 0$  V.

As shown in the graph in Figure 7-5(b), **breakdown** occurs at point *C* when  $I_D$  begins to increase very rapidly with any further increase in  $V_{DS}$ . Breakdown can result in irreversible damage to the device, so JFETs are always operated below breakdown and within the constant-current area (between points *B* and *C* on the graph). The JFET action that produces the drain characteristic curve to the point of breakdown for  $V_{GS} = 0$  V is illustrated in Figure 7-6.

**$V_{GS}$  Controls  $I_D$**

Let's connect a bias voltage,  $V_{GG}$ , from gate to source as shown in Figure 7-7(a). As  $V_{GS}$  is set to increasingly more negative values by adjusting  $V_{GG}$ , a family of drain characteristic curves is produced, as shown in Figure 7-7(b). Notice that  $I_D$  decreases as the magnitude of  $V_{GS}$  is increased to larger negative values because of the narrowing of the channel. Also notice that, for each increase in  $V_{GS}$ , the JFET reaches pinch-off (where constant current begins) at values of  $V_{DS}$  less than  $V_p$ . Therefore, the amount of drain current is controlled by  $V_{GS}$ , as illustrated in Figure 7-8.

 


FIGURE 7-6

JFET action that produces the characteristic curve for  $V_{GS} = 0$  V.

 


FIGURE 7-7

Pinch-off occurs at a lower  $V_{DS}$  as  $V_{GS}$  is increased to more negative values.

 


FIGURE 7-8

$V_{GS}$  controls  $I_D$ .

### Cutoff Voltage

The value of  $V_{GS}$  that makes  $I_D$  approximately zero is the **cutoff voltage**,  $V_{GS(off)}$ . The JFET must be operated between  $V_{GS} = 0\text{ V}$  and  $V_{GS(off)}$ . For this range of gate-to-source voltages,  $I_D$  will vary from a maximum of  $I_{DSS}$  to a minimum of almost zero.

As you have seen, for an  $n$ -channel JFET, the more negative  $V_{GS}$  is, the smaller  $I_D$  becomes in the constant-current area. When  $V_{GS}$  has a sufficiently large negative value,  $I_D$  is reduced to zero. This cutoff effect is caused by the widening of the depletion region to a point where it completely closes the channel, as shown in Figure 7-9.


 


FIGURE 7-9

JFET at cutoff.

The basic operation of a  $p$ -channel JFET is the same as for an  $n$ -channel device except that a  $p$ -channel JFET requires a negative  $V_{DD}$  and a positive  $V_{GS}$ , as illustrated in Figure 7-10.

**FIGURE 7-10**  
A biased  $p$ -channel JFET.

 

### Comparison of Pinch-Off and Cutoff


As you have seen, there is a difference between pinch-off and cutoff. There is also a connection.  $V_P$  is the value of  $V_{DS}$  at which the drain current becomes constant and is always measured at  $V_{GS} = 0$  V. However, pinch-off occurs for  $V_{DS}$  values less than  $V_P$  when  $V_{GS}$  is nonzero. So, although  $V_P$  is a constant, the minimum value of  $V_{DS}$  at which  $I_D$  becomes constant varies with  $V_{GS}$ .

$V_{GS(off)}$  and  $V_P$  are always equal in magnitude but opposite in sign. A data sheet usually will give either  $V_{GS(off)}$  or  $V_P$ , but not both. However, when you know one, you have the other. For example, if  $V_{GS(off)} = -5$  V, then  $V_P = +5$  V, as shown in Figure 7-7(b).

### EXAMPLE 7-1

For the JFET in Figure 7-11,  $V_{GS(off)} = -4$  V and  $I_{DSS} = 12$  mA. Determine the *minimum* value of  $V_{DD}$  required to put the device in the constant-current area of operation.

**FIGURE 7-11**

 

**Solution** Since  $V_{GS(off)} = -4$  V,  $V_P = 4$  V. The minimum value of  $V_{DS}$  for the JFET to be in its constant-current area is

$$V_{DS} = V_P = 4 \text{ V}$$

In the constant-current area with  $V_{GS} = 0$  V,

$$I_D = I_{DSS} = 12 \text{ mA}$$

The drop across the drain resistor is

$$V_{R_D} = I_D R_D = (12 \text{ mA})(560 \Omega) = 6.72 \text{ V}$$

Apply Kirchhoff's law around the drain circuit,

$$V_{DD} = V_{DS} + V_{R_D} = 4 \text{ V} + 6.72 \text{ V} = 10.7 \text{ V}$$

This is the value of  $V_{DD}$  to make  $V_{DS} = V_P$  and put the device in the constant-current area.

*Related Problem*\* If  $V_{DD}$  is increased to 15 V, what is the drain current?

\*Answers are at the end of the chapter.

**EXAMPLE 7-2**


A particular *p*-channel JFET has a  $V_{GS(off)} = +4$  V. What is  $I_D$  when  $V_{GS} = +6$  V?

*Solution* The *p*-channel JFET requires a positive gate-to-source voltage. The more positive the voltage, the less the drain current. When  $V_{GS} = 4$  V,  $I_D = 0$ . Any further increase in  $V_{GS}$  keeps the JFET cut off, so  $I_D$  remains 0.

*Related Problem* What is  $V_P$  for the JFET described in this example?

**JFET Transfer Characteristic**

You have learned that a range of  $V_{GS}$  values from zero to  $V_{GS(off)}$  controls the amount of drain current. For an *n*-channel JFET,  $V_{GS(off)}$  is negative, and for a *p*-channel JFET,  $V_{GS(off)}$  is positive. Because  $V_{GS}$  does control  $I_D$ , the relationship between these two quantities is very important. Figure 7-12 is a general transfer characteristic curve that illustrates graphically the relationship between  $V_{GS}$  and  $I_D$ .

 

**FIGURE 7-12**  
JFET transfer characteristic curve  
(*n*-channel).


Notice that the bottom end of the curve is at a point on the  $V_{GS}$  axis equal to  $V_{GS(off)}$ , and the top end of the curve is at a point on the  $I_D$  axis equal to  $I_{DSS}$ . This curve, of course, shows that the operating limits of a JFET are

$$I_D = 0 \quad \text{when } V_{GS} = V_{GS(off)}$$

and

$$I_D = I_{DSS} \quad \text{when } V_{GS} = 0$$

The transfer characteristic curve can be developed from the drain characteristic curves by plotting values of  $I_D$  for the values of  $V_{GS}$  taken from the family of drain curves at pinch-off, as illustrated in Figure 7-13 for a specific set of curves. Each point on the transfer characteristic curve corresponds to specific values of  $V_{GS}$  and  $I_D$  on the drain curves. For

 

**FIGURE 7-13**  
 Example of the development of an *n*-channel JFET transfer characteristic curve (blue) from the JFET drain characteristic curves (green).

example, when  $V_{GS} = -2\text{ V}$ ,  $I_D = 4.32\text{ mA}$ . Also, for this specific JFET,  $V_{GS(off)} = -5\text{ V}$  and  $I_{DSS} = 12\text{ mA}$ .

A JFET transfer characteristic curve is expressed as

Equation 7-1 
$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2$$

With Equation 7-1,  $I_D$  can be determined for any  $V_{GS}$  if  $V_{GS(off)}$  and  $I_{DSS}$  are known. These quantities are usually available from the data sheet for a given JFET. Notice the squared term in the equation. Because of its form, a parabolic relationship is known as a *square law*, and therefore, JFETs and MOSFETs are often referred to as *square-law devices*. The data sheet for a typical JFET series is shown in Figure 7-14.

**EXAMPLE 7-3**

The partial data sheet in Figure 7-14 for a 2N5459 JFET indicates that typically  $I_{DSS} = 9\text{ mA}$  and  $V_{GS(off)} = -8\text{ V}$  (maximum). Using these values, determine the drain current for  $V_{GS} = 0\text{ V}$ ,  $-1\text{ V}$ , and  $-4\text{ V}$ .

**Solution** For  $V_{GS} = 0\text{ V}$ ,

$$I_D = I_{DSS} = 9\text{ mA}$$

For  $V_{GS} = -1\text{ V}$ , use Equation 7-1.

$$\begin{aligned} I_D &= I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2 = (9\text{ mA}) \left( 1 - \frac{-1\text{ V}}{-8\text{ V}} \right)^2 \\ &= (9\text{ mA})(1 - 0.125)^2 = (9\text{ mA})(0.766) = 6.89\text{ mA} \end{aligned}$$

For  $V_{GS} = -4\text{ V}$ ,

$$I_D = (9\text{ mA}) \left( 1 - \frac{-4\text{ V}}{-8\text{ V}} \right)^2 = (9\text{ mA})(1 - 0.5)^2 = (9\text{ mA})(0.25) = 2.25\text{ mA}$$


*Related Problem* Determine  $I_D$  for  $V_{GS} = -3\text{ V}$  for the 2N5459 JFET.

Maximum Ratings

Rating	Symbol	Value	Unit
Drain-Source voltage	$V_{DS}$	25	V dc
Drain-Gate voltage	$V_{DG}$	25	V dc
Reverse gate-source voltage	$V_{GSR}$	-25	V dc
Gate current	$I_G$	10	mA dc
Total device dissipation @ $T_A = 25^\circ\text{C}$ Derate above $25^\circ\text{C}$	$P_D$	310 2.82	mW mW/°C
Junction temperature	$T_J$	125	°C
Storage channel temperature range	$T_{stg}$	-65 to +150	°C

**2N5457  
thru  
2N5459**

Case 29-04, Style 5  
TO-92 (TO-226AA)

 **JFETs**  
**General-Purpose**  
N channel — Depletion

Electrical Characteristics ( $T_A = 25^\circ\text{C}$  unless otherwise noted.)

Characteristic	Symbol	Min	Typ	Max	Unit
<b>OFF Characteristics</b>					
Gate-Source breakdown voltage ( $I_G = -10\ \mu\text{A}$ dc, $V_{DS} = 0$ )	$V_{(BR)GSS}$	-25	-	-	V dc
Gate reverse current ( $V_{GS} = -15\text{ V}$ dc, $V_{DS} = 0$ ) ( $V_{GS} = -15\text{ V}$ dc, $V_{DS} = 0$ , $T_A = 100^\circ\text{C}$ )	$I_{OSS}$	-	-	-1.0 -200	nA dc
Gate-Source cutoff voltage ( $V_{DS} = 15\text{ V}$ dc, $I_D = 10\text{ nA}$ dc)	$V_{GS(off)}$	-0.5 -1.0 -2.0	-	-6.0 -7.0 -8.0	V dc
Gate-Source voltage ( $V_{DS} = 15\text{ V}$ dc, $I_D = 100\ \mu\text{A}$ dc) ( $V_{DS} = 15\text{ V}$ dc, $I_D = 200\ \mu\text{A}$ dc) ( $V_{DS} = 15\text{ V}$ dc, $I_D = 400\ \mu\text{A}$ dc)	$V_{GS}$	-	-2.5 -3.5 -4.5	-	V dc
<b>ON Characteristics</b>					
Zero-Gate-Voltage drain current ( $V_{DS} = 15\text{ V}$ dc, $V_{GS} = 0$ )	$I_{DSS}$	1.0 2.0 4.0	3.0 6.0 9.0	5.0 9.0 16	mA dc
<b>Small-signal Characteristics</b>					
Forward transfer admittance common source ( $V_{DS} = 15\text{ V}$ dc, $V_{GS} = 0$ , $f = 1.0\text{ kHz}$ )	$ y_{fs} $	1000 1500 2000	-	5000 5500 6000	$\mu\text{mhos}$ or $\mu\text{S}$
Output admittance common source ( $V_{DS} = 15\text{ V}$ dc, $V_{GS} = 0$ , $f = 1.0\text{ kHz}$ )	$ y_{os} $	-	10	50	$\mu\text{mhos}$ or $\mu\text{S}$
Input capacitance ( $V_{DS} = 15\text{ V}$ dc, $V_{GS} = 0$ , $f = 1.0\text{ MHz}$ )	$C_{iss}$	-	4.5	7.0	pF
Reverse transfer capacitance ( $V_{DS} = 15\text{ V}$ dc, $V_{GS} = 0$ , $f = 1.0\text{ MHz}$ )	$C_{rss}$	-	1.5	3.0	pF

FIGURE 7-14

JFET partial data sheet.

### JFET Forward Transconductance



The forward transconductance (transfer conductance),  $g_m$ , is the change in drain current ( $\Delta I_D$ ) for a given change in gate-to-source voltage ( $\Delta V_{GS}$ ) with the drain-to-source voltage constant. It is expressed as a ratio and has the unit of siemens (S).


$$g_m = \frac{\Delta I_D}{\Delta V_{GS}}$$

Other common designations for this parameter are  $g_{fs}$  and  $y_{fs}$  (forward transfer admittance). As you will see in Chapter 8,  $g_m$  is important in FET amplifiers as a major factor in determining the voltage gain.

Because the transfer characteristic curve for a JFET is nonlinear,  $g_m$  varies in value depending on the location on the curve as set by  $V_{GS}$ . The value for  $g_m$  is greater near the top of the curve (near  $V_{GS} = 0$ ) than it is near the bottom (near  $V_{GS(off)}$ ), as illustrated in Figure 7-15.

FIGURE 7-15

 $g_m$  varies depending on the bias point ( $V_{GS}$ ).



A data sheet normally gives the value of  $g_m$  measured at  $V_{GS} = 0$  V ( $g_{m0}$ ). For example, the data sheet for the 2N5457 JFET specifies a minimum  $g_{m0}$  ( $y_{fs}$ ) of 1000 S with  $V_{DS} = 15$  V.

Given  $g_{m0}$ , you can calculate an approximate value for  $g_m$  at any point on the transfer characteristic curve using the following formula:

Equation 7-2

$$g_m = g_{m0} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)$$

When a value of  $g_{m0}$  is not available, you can calculate it using values of  $I_{DSS}$  and  $V_{GS(off)}$ . The vertical lines indicate an absolute value (no sign).

Equation 7-3

$$g_{m0} = \frac{2I_{DSS}}{|V_{GS(off)}|}$$

#### EXAMPLE 7-4

The following information is included on the data sheet in Figure 7-14 for a 2N5457 JFET: typically,  $I_{DSS} = 3.0$  mA,  $V_{GS(off)} = -6$  V maximum, and  $y_{fs(max)} = 5000$   $\mu$ S. Using these values, determine the forward transconductance for  $V_{GS} = -4$  V, and find  $I_D$  at this point.

*Solution*  $g_{m0} = y_{fs} = 5000 \mu\text{S}$ . Use Equation 7-2 to calculate  $g_m$ .

$$g_m = g_{m0} \left( 1 - \frac{V_{GS}}{V_{GS(\text{off})}} \right) = (5000 \mu\text{S}) \left( 1 - \frac{-4 \text{ V}}{-6 \text{ V}} \right) = 1667 \mu\text{S}$$

Next, use Equation 7-1 to calculate  $I_D$  at  $V_{GS} = -4 \text{ V}$ .

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(\text{off})}} \right)^2 = (3.0 \text{ mA}) \left( 1 - \frac{-4 \text{ V}}{-6 \text{ V}} \right)^2 = 333 \mu\text{A}$$

*Related Problem* A given JFET has the following characteristics:  $I_{DSS} = 12 \text{ mA}$ ,  $V_{GS(\text{off})} = -5 \text{ V}$ , and  $g_{m0} = 3000 \mu\text{S}$ . Find  $g_m$  and  $I_D$  when  $V_{GS} = -2 \text{ V}$ .

### Input Resistance and Capacitance

As you know, a JFET operates with its gate-source junction reverse-biased, which makes the input resistance at the gate very high. This high input resistance is one advantage of the JFET over the BJT. (Recall that a bipolar junction transistor operates with a forward-biased base-emitter junction.) JFET data sheets often specify the input resistance by giving a value for the gate reverse current,  $I_{GSS}$ , at a certain gate-to-source voltage. The input resistance can then be determined using the following equation, where the vertical lines indicate an absolute value (no sign):

$$R_{IN} = \frac{|V_{GS}|}{|I_{GSS}|}$$

For example, the 2N5457 data sheet in Figure 7-14 lists a maximum  $I_{GSS}$  of  $-1.0 \text{ nA}$  for  $V_{GS} = -15 \text{ V}$  at  $25^\circ\text{C}$ .  $I_{GSS}$  increases with temperature, so the input resistance decreases.

The input capacitance,  $C_{iss}$ , is a result of the JFET operating with a reverse-biased  $pn$  junction. Recall that a reverse-biased  $pn$  junction acts as a capacitor whose capacitance depends on the amount of reverse voltage. For example, the 2N5457 has a maximum  $C_{iss}$  of  $7 \text{ pF}$  for  $V_{GS} = 0$ .

#### EXAMPLE 7-5

A certain JFET has an  $I_{GSS}$  of  $-2 \text{ nA}$  for  $V_{GS} = -20 \text{ V}$ . Determine the input resistance.

*Solution*

$$R_{IN} = \frac{|V_{GS}|}{|I_{GSS}|} = \frac{20 \text{ V}}{2 \text{ nA}} = 10,000 \text{ M}\Omega$$

*Related Problem* Determine the minimum input resistance for the 2N5458 from the data sheet in Figure 7-14.

### Drain-to-Source Resistance

You learned from the drain characteristic curve that, above pinch-off, the drain current is relatively constant over a range of drain-to-source voltages. Therefore, a large change in  $V_{DS}$  produces only a very small change in  $I_D$ . The ratio of these changes is the drain-to-source resistance of the device,  $r'_{ds}$ .

$$r'_{ds} = \frac{\Delta V_{DS}}{\Delta I_D}$$

Data sheets often specify this parameter in terms of the output conductance,  $g_{os}$ , or output admittance,  $y_{os}$ .

### SECTION 7-2 REVIEW

1. The drain-to-source voltage at the pinch-off point of a particular JFET is 7 V. If the gate-to-source voltage is zero, what is  $V_p$ ?
2. The  $V_{GS}$  of a certain  $n$ -channel JFET is increased negatively. Does the drain current increase or decrease?
3. What value must  $V_{GS}$  have to produce cutoff in a  $p$ -channel JFET with a  $V_p = -3$  V?

## 7-3 JFET BIASING

Using some of the FET parameters discussed in the previous sections, you will now see how to dc-bias JFETs. Just as with the BJT, the purpose of biasing is to select the proper dc gate-to-source voltage to establish a desired value of drain current and, thus, a proper Q-point. You will learn about two types of bias circuits, self-bias and voltage-divider bias.


After completing this section, you should be able to

- Discuss and analyze JFET bias circuits
- Describe self-bias
- Analyze a self-biased JFET circuit
- Set the self-biased Q-point
- Analyze a JFET circuit with voltage-divider bias
- Use transfer characteristic curves to analyze JFET bias circuits
- Discuss Q-point stability

### Self-Bias

Self-bias is the most common type of JFET bias. Recall that a JFET must be operated such that the gate-source junction is always reverse-biased. This condition requires a negative  $V_{GS}$  for an  $n$ -channel JFET and a positive  $V_{GS}$  for a  $p$ -channel JFET. This can be achieved using the self-bias arrangements shown in Figure 7-16. The gate resistor,  $R_G$ , does not affect the bias because it has essentially no voltage drop across it; and therefore the gate remains at 0 V.  $R_G$  is necessary only to isolate an ac signal from ground in amplifier applications, as you will see later.

FIGURE 7-16  
Self-biased JFETs ( $I_S = I_D$  in all FETs).

 

For the *n*-channel JFET in Figure 7-16(a),  $I_S$  produces a voltage drop across  $R_S$  and makes the source positive with respect to ground. Since  $I_S = I_D$  and  $V_G = 0$ , then  $V_S = I_D R_S$ . The gate-to-source voltage is

$$V_{GS} = V_G - V_S = 0 - I_D R_S = -I_D R_S$$

Thus,

$$V_{GS} = -I_D R_S$$

For the *p*-channel JFET shown in Figure 7-16(b), the current through  $R_S$  produces a negative voltage at the source, making the gate positive with respect to the source. Therefore, since  $I_S = I_D$ ,

$$V_{GS} = +I_D R_S$$

In the following analysis, the *n*-channel JFET in Figure 7-16(a) is used for illustration. Keep in mind that analysis of the *p*-channel JFET is the same except for opposite-polarity voltages. The drain voltage with respect to ground is determined as follows:

$$V_D = V_{DD} - I_D R_D$$


Since  $V_S = I_D R_S$ , the drain-to-source voltage is

$$V_{DS} = V_D - V_S = V_{DD} - I_D (R_D + R_S)$$

**EXAMPLE 7-6**

Find  $V_{DS}$  and  $V_{GS}$  in Figure 7-17. For the particular JFET in this circuit, the internal parameter values such as  $g_m$ ,  $V_{GS(off)}$ , and  $I_{DSS}$  are such that a drain current ( $I_D$ ) of approximately 5 mA is produced. Another JFET, even of the same type, may not produce the same results when connected in this circuit due to the variations in parameter values.

**FIGURE 7-17**

 

*Solution*

$$V_S = I_D R_S = (5 \text{ mA})(220 \Omega) = 1.1 \text{ V}$$

$$V_D = V_{DD} - I_D R_D = 15 \text{ V} - (5 \text{ mA})(1.0 \text{ k}\Omega) = 15 \text{ V} - 5 \text{ V} = 10 \text{ V}$$

Therefore,

$$V_{DS} = V_D - V_S = 10 \text{ V} - 1.1 \text{ V} = 8.9 \text{ V}$$

Since  $V_G = 0 \text{ V}$ ,

$$V_{GS} = V_G - V_S = 0 \text{ V} - 1.1 \text{ V} = -1.1 \text{ V}$$

**Related Problem** Determine  $V_{DS}$  and  $V_{GS}$  in Figure 7-17 when  $I_D = 8 \text{ mA}$ . Assume that  $R_D = 860 \Omega$ ,  $R_S = 390 \Omega$ , and  $V_{DD} = 12 \text{ V}$ .



Open the Multisim file E07-06 in the Examples folder on your CD-ROM. Measure  $I_D$ ,  $V_{GS}$ , and  $V_{DS}$  and compare to the calculated values from the Related Problem.

### Setting the Q-Point of a Self-Biased JFET

The basic approach to establishing a JFET bias point is to determine  $I_D$  for a desired value of  $V_{GS}$  or vice versa. Then calculate the required value of  $R_S$  using the following relationship. The vertical lines indicate an absolute value.


$$R_S = \left| \frac{V_{GS}}{I_D} \right|$$

For a desired value of  $V_{GS}$ ,  $I_D$  can be determined in either of two ways: from the transfer characteristic curve for the particular JFET or, more practically, from Equation 7-1 using  $I_{DSS}$  and  $V_{GS(off)}$  from the JFET data sheet. The next two examples illustrate these procedures.

#### EXAMPLE 7-7

Determine the value of  $R_S$  required to self-bias an  $n$ -channel JFET that has the transfer characteristic curve shown in Figure 7-18 at  $V_{GS} = -5 \text{ V}$ .

FIGURE 7-18

 

**Solution** From the graph,  $I_D = 6.25 \text{ mA}$  when  $V_{GS} = -5 \text{ V}$ . Calculate  $R_S$ .

$$R_S = \left| \frac{V_{GS}}{I_D} \right| = \frac{5 \text{ V}}{6.25 \text{ mA}} = 800 \Omega$$

**Related Problem** Find  $R_S$  for  $V_{GS} = -3 \text{ V}$ .

**EXAMPLE 7-8**

Determine the value of  $R_S$  required to self-bias a p-channel JFET with  $I_{DSS} = 25 \text{ mA}$  and  $V_{GS(off)} = 15 \text{ V}$ .  $V_{GS}$  is to be  $5 \text{ V}$ .

**Solution** Use Equation 7-1 to calculate  $I_D$ .

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2 = (25 \text{ mA}) \left( 1 - \frac{5 \text{ V}}{15 \text{ V}} \right)^2$$

$$= (25 \text{ mA})(1 - 0.333)^2 = 11.1 \text{ mA}$$

Now, determine  $R_S$ .

$$R_S = \left| \frac{V_{GS}}{I_D} \right| = \frac{5 \text{ V}}{11.1 \text{ mA}} = 450 \Omega$$

**Related Problem** Find the value of  $R_S$  required to self-bias a p-channel JFET with  $I_{DSS} = 18 \text{ mA}$  and  $V_{GS(off)} = 8 \text{ V}$ .  $V_{GS} = 4 \text{ V}$ .

**Midpoint Bias** It is usually desirable to bias a JFET near the midpoint of its transfer characteristic curve where  $I_D = I_{DSS}/2$ . Under signal conditions, midpoint bias allows the maximum amount of drain current swing between  $I_{DSS}$  and 0. Using Equation 7-1, it is shown in Appendix B that  $I_D$  is approximately one-half of  $I_{DSS}$  when  $V_{GS} = V_{GS(off)}/3.4$ .

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2 = I_{DSS} \left( 1 - \frac{V_{GS(off)}/3.4}{V_{GS(off)}} \right)^2 = 0.5I_{DSS}$$


So, by selecting  $V_{GS} = V_{GS(off)}/3.4$ , you should get a midpoint bias in terms of  $I_D$ .

To set the drain voltage at midpoint ( $V_D = V_{DD}/2$ ), select a value of  $R_D$  to produce the desired voltage drop. Choose  $R_G$  arbitrarily large to prevent loading on the driving stage in a cascaded amplifier arrangement. Example 7-9 illustrates these concepts.

**EXAMPLE 7-9**

Select resistor values for  $R_D$  and  $R_S$  in Figure 7-19 to set up an approximate midpoint bias. For this particular JFET, the parameters are  $I_{DSS} = 12 \text{ mA}$  and  $V_{GS(off)} = -3 \text{ V}$ .  $V_D$  should be approximately  $6 \text{ V}$  (one-half of  $V_{DD}$ ).

**FIGURE 7-19**

 

**Solution** For midpoint bias,

$$I_D \cong \frac{I_{DSS}}{2} = 6 \text{ mA}$$

and

$$V_{GS} \cong \frac{V_{GS(off)}}{3.4} = \frac{-3 \text{ V}}{3.4} = -882 \text{ mV}$$

Then

$$R_S = \left| \frac{V_{GS}}{I_D} \right| = \frac{882 \text{ mV}}{6 \text{ mA}} = 147 \Omega$$

$$V_D = V_{DD} - I_D R_D$$

$$I_D R_D = V_{DD} - V_D$$

$$R_D = \frac{V_{DD} - V_D}{I_D} = \frac{12 \text{ V} - 6 \text{ V}}{6 \text{ mA}} = 1 \text{ k}\Omega$$

**Related Problem** Select resistor values in Figure 7-19 to set up an approximate midpoint bias. The JFET parameters are  $I_{DSS} = 10 \text{ mA}$  and  $V_{GS(off)} = -10 \text{ V}$ .  $V_{DD} = 15 \text{ V}$ .





Open the Multisim file E07-09 in the Examples folder on your CD-ROM. The circuit has the calculated values for  $R_D$  and  $R_S$  from the Related Problem. Verify that an approximate midpoint bias is established by measuring  $V_D$  and  $I_D$ .

### Graphical Analysis of a Self-Biased JFET

You can use the transfer characteristic curve of a JFET and certain parameters to determine the Q-point ( $I_D$  and  $V_{GS}$ ) of a self-biased circuit. A circuit is shown in Figure 7-20(a), and a transfer characteristic curve is shown in Figure 7-20(b). If a curve is not available from a data sheet, you can plot it from Equation 7-1 using data sheet values for  $I_{DSS}$  and  $V_{GS(off)}$ .

**FIGURE 7-20**  
A self-biased JFET and its transfer characteristic curve.

  

To determine the Q-point of the circuit in Figure 7-20(a), a self-bias dc load line is established on the graph in part (b) as follows. First, calculate  $V_{GS}$  when  $I_D$  is zero.

$$V_{GS} = -I_D R_S = (0)(470 \Omega) = 0 \text{ V}$$

This establishes a point at the origin on the graph ( $I_D = 0$ ,  $V_{GS} = 0$ ). Next, calculate  $V_{GS}$  when  $I_D = I_{DSS}$ . From the curve in Figure 7-20(b),  $I_{DSS} = 10 \text{ mA}$ .

$$V_{GS} = -I_D R_S = -(10 \text{ mA})(470 \Omega) = -4.7 \text{ V}$$

This establishes a second point on the graph ( $I_D = 10 \text{ mA}$ ,  $V_{GS} = -4.7 \text{ V}$ ). Now, with two points, the load line can be drawn on the transfer characteristic curve as shown in Figure 7-21. The point where the line intersects the transfer characteristic curve is the Q-point of the circuit as shown.

 




FIGURE 7-21

The intersection of the self-bias dc load line and the transfer characteristic curve is the Q-point.

**EXAMPLE 7-10**

Determine the Q-point for the JFET circuit in Figure 7-22(a). The transfer characteristic curve is given in Figure 7-22(b).

FIGURE 7-22

  

**Solution** For  $I_D = 0$ ,

$$V_{GS} = -I_D R_S = (0)(680 \Omega) = 0 \text{ V}$$

This gives a point at the origin. From the curve,  $I_{DSS} = 4 \text{ mA}$ ; so  $I_D = I_{DSS} = 4 \text{ mA}$ .

$$V_{GS} = -I_D R_S = -(4 \text{ mA})(680 \Omega) = -2.72 \text{ V}$$

This gives a second point at 4 mA and  $-2.72 \text{ V}$ . A line is now drawn between the two points, and the values of  $I_D$  and  $V_{GS}$  at the intersection of the line and the curve are taken from the graph, as illustrated in Figure 7-22(b). The Q-point values from the graph are

$$I_D = 2.25 \text{ mA}$$

$$V_{GS} = -1.5 \text{ V}$$


**Related Problem** If  $R_S$  is increased to  $1.0 \text{ k}\Omega$  in Figure 7-22(a), what is the new Q-point?

### Voltage-Divider Bias

An *n*-channel JFET with voltage-divider bias is shown in Figure 7-23. The voltage at the source of the JFET must be more positive than the voltage at the gate in order to keep the gate-source junction reverse-biased.

**FIGURE 7-23**

 An *n*-channel JFET with voltage-divider bias ( $I_S = I_D$ ).



The source voltage is

$$V_S = I_D R_S$$

The gate voltage is set by resistors  $R_1$  and  $R_2$  as expressed by the following equation using the voltage-divider formula:

$$V_G = \left( \frac{R_2}{R_1 + R_2} \right) V_{DD}$$

The gate-to-source voltage is

$$V_{GS} = V_G - V_S$$

and the source voltage is

$$V_S = V_G - V_{GS}$$

The drain current can be expressed as

$$I_D = \frac{V_S}{R_S}$$


Substituting for  $V_S$ ,

$$I_D = \frac{V_G - V_{GS}}{R_S}$$

**EXAMPLE 7-11**

Determine  $I_D$  and  $V_{GS}$  for the JFET with voltage-divider bias in Figure 7-24, given that for this particular JFET the internal parameter values are such that  $V_D \cong 7$  V.

FIGURE 7-24

 

**Solution**

$$I_D = \frac{V_{DD} - V_D}{R_D} = \frac{12 \text{ V} - 7 \text{ V}}{3.3 \text{ k}\Omega} = \frac{5 \text{ V}}{3.3 \text{ k}\Omega} = 1.52 \text{ mA}$$

Calculate the gate-to-source voltage as follows:

$$V_S = I_D R_S = (1.52 \text{ mA})(2.2 \text{ k}\Omega) = 3.34 \text{ V}$$

$$V_G = \left( \frac{R_2}{R_1 + R_2} \right) V_{DD} = \left( \frac{1.0 \text{ M}\Omega}{7.8 \text{ M}\Omega} \right) 12 \text{ V} = 1.54 \text{ V}$$

$$V_{GS} = V_G - V_S = 1.54 \text{ V} - 3.34 \text{ V} = -1.8 \text{ V}$$

If  $V_D$  had not been given in this example, the Q-point values could not have been found without the transfer characteristic curve.

**Related Problem** Given that  $V_D = 6$  V when another JFET is inserted in the circuit of Figure 7-24, determine the Q-point.

**Graphical Analysis of a JFET with Voltage-Divider Bias**

An approach similar to the one used for self-bias can be used with voltage-divider bias to graphically determine the Q-point of a circuit on the transfer characteristic curve.

In a JFET with voltage-divider bias when  $I_D = 0$ ,  $V_{GS}$  is not zero, as in the self-biased case, because the voltage divider produces a voltage at the gate independent of the drain current. The voltage-divider dc load line is determined as follows.

For  $I_D = 0$ ,

$$V_S = I_D R_S = (0)R_S = 0 \text{ V}$$

$$V_{GS} = V_G - V_S = V_G - 0 \text{ V} = V_G$$

Therefore, one point on the line is at  $I_D = 0$  and  $V_{GS} = V_G$ .


For  $V_{GS} = 0$ ,

$$I_D = \frac{V_G - V_{GS}}{R_S} = \frac{V_G}{R_S}$$

A second point on the line is at  $I_D = V_G/R_S$  and  $V_{GS} = 0$ . The generalized dc load line is shown in Figure 7-25. The point at which the load line intersects the transfer characteristic curve is the Q-point.

FIGURE 7-25

Generalized dc load line for a JFET with voltage-divider bias.

 

**EXAMPLE 7-12**

Determine the approximate Q-point for the JFET with voltage-divider bias in Figure 7-26(a), given that this particular device has a transfer characteristic curve as shown in Figure 7-26(b).

 


FIGURE 7-26

*Solution* First, establish the two points for the bias line. For  $I_D = 0$ ,

$$V_{GS} = V_G = \left( \frac{R_2}{R_1 + R_2} \right) V_{DD} = \left( \frac{2.2 \text{ M}\Omega}{4.4 \text{ M}\Omega} \right) 8 \text{ V} = 4 \text{ V}$$

The first point is at  $I_D = 0$  and  $V_{GS} = 4 \text{ V}$ . For  $V_{GS} = 0$ ,

$$I_D = \frac{V_G - V_{GS}}{R_S} = \frac{V_G}{R_S} = \frac{4 \text{ V}}{3.3 \text{ k}\Omega} = 1.2 \text{ mA}$$

The second point is at  $I_D = 1.2 \text{ mA}$  and  $V_{GS} = 0$ .

The load line is drawn in Figure 7-26(b), and the approximate Q-point values of  $I_D \cong 1.8 \text{ mA}$  and  $V_{GS} \cong -1.8 \text{ V}$  are picked off the graph, as indicated.

*Related Problem* Change  $R_S$  to  $4.7 \text{ k}\Omega$  and determine the Q-point for the circuit in Figure 7-26(a).



Open the Multisim file E07-12 in the Examples folder on your CD-ROM. Measure the Q-point values of  $I_D$  and  $V_{GS}$  and see how they compare to the graphically determined values from the Related Problem.

### Q-Point Stability

Unfortunately, the transfer characteristic of a JFET can differ considerably from one device to another of the same type. If, for example, a 2N5459 JFET is replaced in a given bias circuit with another 2N5459, the transfer characteristic curve can vary greatly, as illustrated in Figure 7-27(a). In this case, the maximum  $I_{DSS}$  is  $16 \text{ mA}$  and the minimum  $I_{DSS}$  is  $4 \text{ mA}$ . Likewise, the maximum  $V_{GS(off)}$  is  $-8 \text{ V}$  and the minimum  $V_{GS(off)}$  is  $-2 \text{ V}$ . This means that if you have a selection of 2N5459s and you randomly pick one out, it can have values anywhere within these ranges.

 


FIGURE 7-27

Variation in the transfer characteristic of 2N5459 JFETs and the effect on the Q-point.

If a self-bias dc load line is drawn as illustrated in Figure 7-27(b), the same circuit using a 2N5459 can have a Q-point anywhere along the line from  $Q_1$ , the minimum bias point, to  $Q_2$ , the maximum bias point. Accordingly, the drain current can be any value between  $I_{D1}$  and  $I_{D2}$ , as shown by the shaded area. This means that the dc voltage at the drain can have a range of values depending on  $I_D$ . Also, the gate-to-source voltage can be any value between  $V_{GS1}$  and  $V_{GS2}$ , as indicated.

Figure 7-28 illustrates Q-point stability for a self-biased JFET and for a JFET with voltage-divider bias. With voltage-divider bias, the dependency of  $I_D$  on the range of Q-points is reduced because the slope of the bias line is less than for self-bias. Although  $V_{GS}$  varies quite a bit for both self-bias and voltage-divider bias,  $I_D$  is much more stable with voltage-divider bias.

 


FIGURE 7-28

The change in  $I_D$  between the minimum and the maximum Q-points is much less for a JFET with voltage-divider bias than for a self-biased JFET.

**SECTION 7-3**  
**REVIEW**

1. Should a *p*-channel JFET have a positive or a negative  $V_{GS}$ ?
2. In a certain self-biased *n*-channel JFET circuit,  $I_D = 8 \text{ mA}$  and  $R_S = 1.0 \text{ k}\Omega$ . Determine  $V_{GS}$ .
3. An *n*-channel JFET with voltage-divider bias has a gate voltage of 3 V and a source voltage of 5 V. Calculate  $V_{GS}$ .

**7-4 THE MOSFET**

The MOSFET (metal oxide semiconductor field-effect transistor) is another category of field-effect transistor. The MOSFET differs from the JFET in that it has no *pn* junction structure; instead, the gate of the MOSFET is insulated from the channel by a silicon dioxide ( $\text{SiO}_2$ ) layer. The two basic types of MOSFETs are

depletion (D) and enhancement (E). Because of the insulated gate, these devices are sometimes called IGFETs.

After completing this section, you should be able to

- Explain the operation of MOSFETs
- Describe the structural difference between an  $n$ -channel and a  $p$ -channel depletion MOSFET (D-MOSFET)
- Explain the depletion mode
- Explain the enhancement mode
- Identify the symbols for  $n$ -channel and  $p$ -channel D-MOSFETs
- Describe the structural difference between an  $n$ -channel and a  $p$ -channel enhancement MOSFET (E-MOSFET)
- Identify the symbols for  $n$ -channel and  $p$ -channel E-MOSFETs
- Explain how D-MOSFETs and E-MOSFETs differ
- Discuss power MOSFETs
- Discuss dual-gate MOSFETs

### Depletion MOSFET (D-MOSFET)

One type of MOSFET is the depletion MOSFET (D-MOSFET), and Figure 7-29 illustrates its basic structure. The drain and source are diffused into the substrate material and then connected by a narrow channel adjacent to the insulated gate. Both  $n$ -channel and  $p$ -channel devices are shown in the figure. We will use the  $n$ -channel device to describe the basic operation. The  $p$ -channel operation is the same, except the voltage polarities are opposite those of the  $n$ -channel.

 


FIGURE 7-29

Representation of the basic structure of D-MOSFETs.

The D-MOSFET can be operated in either of two modes—the depletion mode or the enhancement mode—and is sometimes called a *depletion/enhancement MOSFET*. Since the gate is insulated from the channel, either a positive or a negative gate voltage can be applied. The  $n$ -channel MOSFET operates in the **depletion** mode when a negative gate-to-source voltage is applied and in the **enhancement** mode when a positive gate-to-source voltage is applied. These devices are generally operated in the depletion mode.

**Depletion Mode** Visualize the gate as one plate of a parallel-plate capacitor and the channel as the other plate. The silicon dioxide insulating layer is the dielectric. With a negative gate voltage, the negative charges on the gate repel conduction electrons from the channel, leaving positive ions in their place. Thereby, the  $n$  channel is depleted of some of its electrons, thus decreasing the channel conductivity. The greater the negative voltage on the gate, the greater the depletion of  $n$ -channel electrons. At a sufficiently negative gate-to-source voltage,  $V_{GS(off)}$ , the channel is totally depleted and the drain current is zero. This depletion mode is illustrated in Figure 7-30(a). Like the  $n$ -channel JFET, the  $n$ -channel D-MOSFET conducts drain current for gate-to-source voltages between  $V_{GS(off)}$  and zero. In addition, the D-MOSFET conducts for values of  $V_{GS}$  above zero.

 


FIGURE 7-30


Operation of  $n$ -channel D-MOSFET.

**Enhancement Mode** With a positive gate voltage, more conduction electrons are attracted into the channel, thus increasing (enhancing) the channel conductivity, as illustrated in Figure 7-30(b).

**D-MOSFET Symbols** The schematic symbols for both the  $n$ -channel and the  $p$ -channel depletion MOSFETs are shown in Figure 7-31. The substrate, indicated by the arrow, is normally (but not always) connected internally to the source. Sometimes, there is a separate substrate pin. An inward-pointing substrate arrow is for  $n$  channel, and an outward-pointing arrow is for  $p$  channel.

FIGURE 7-31

D-MOSFET schematic symbols.

 

### Enhancement MOSFET (E-MOSFET)

The E-MOSFET operates *only* in the enhancement mode and has no depletion mode. It differs in construction from the D-MOSFET in that it has no structural channel. Notice in Figure 7-32(a) that the substrate extends completely to the SiO<sub>2</sub> layer. For an *n*-channel device, a positive gate voltage above a threshold value *induces* a channel by creating a thin layer of negative charges in the substrate region adjacent to the SiO<sub>2</sub> layer, as shown in Figure 7-32(b). The conductivity of the channel is enhanced by increasing the gate-to-source voltage and thus pulling more electrons into the channel area. For any gate voltage below the threshold value, there is no channel.

 


FIGURE 7-32

Representation of the basic E-MOSFET construction and operation (*n*-channel).

The schematic symbols for the *n*-channel and *p*-channel E-MOSFETs are shown in Figure 7-33. The broken lines symbolize the absence of a physical channel. Like the D-MOSFET, some devices have a separate substrate connection.

 



FIGURE 7-33  
E-MOSFET schematic symbols.

### Power MOSFETs

The conventional enhancement MOSFETs have a long thin lateral channel as shown in the structural view in Figure 7-34. This results in a relatively high drain-to-source resistance and limits the E-MOSFET to low power applications. When the gate is positive, the channel is formed close to the gate between the source and the drain, as shown.

FIGURE 7-34

 Cross section of conventional E-MOSFET structure. Channel is shown as white area.




**Lateral Double Diffused MOSFET (LDMOSFET)** The LDMOSFET is a type of enhancement MOSFET designed for power applications. This device has a shorter channel between drain and source than does the conventional E-MOSFET. The shorter channel results in lower resistance, which allows higher current and voltage.

Figure 7-35 shows the basic structure of an LDMOSFET. When the gate is positive, a very short  $n$  channel is induced in the  $p$  layer between the lightly doped source and the  $n^-$  region. There is current to the drain through the  $n$  regions and the induced channel from the source, as indicated.

FIGURE 7-35

Cross section of LDMOSFET structure.

 


**VMOSFET** The V-groove MOSFET is another variation of the conventional E-MOSFET designed to achieve higher power capability by creating a shorter and wider channel with less resistance between the drain and source. The shorter, wider channels allow for higher currents and, thus, greater power dissipation. Frequency response is also improved.

The VMOSFET has two source connections, a gate connection on top, and a drain connection on the bottom, as shown in Figure 7-36. The channel is induced vertically along both sides of the V-shaped groove between the drain ( $n^+$  substrate where  $n^+$  means a higher doping level than  $n^-$ ) and the source connections. The channel length is set by the thickness of the layers, which is controlled by doping densities and diffusion time rather than by mask dimensions.

FIGURE 7-36

Cross section of VMOSFET structure.

 

**TMOSFET** TMOSFET is similar to VMOSFET except that it doesn't use a V-shaped groove and is, therefore, easier to manufacture. The structure of TMOSFET is illustrated in Figure 7-37. The gate structure is embedded in a silicon dioxide layer, and the source con-

 


FIGURE 7-37  
Cross section of T MOSFET structure.

fact is continuous over the entire surface area. The drain is on the bottom. T MOSFET achieves greater packing density than V MOSFET, while retaining the short vertical channel advantage.

### Dual-Gate MOSFETs

The dual-gate MOSFET can be either a depletion or an enhancement type. The only difference is that it has two gates, as shown in Figure 7-38. As previously mentioned, one drawback of a FET is its high input capacitance, which restricts its use at higher frequencies. By using a dual-gate device, the input capacitance is reduced, thus making the device useful in high-frequency RF amplifier applications. Another advantage of the dual-gate arrangement is that it allows for an automatic gain control (AGC) input in certain RF amplifiers.

 


FIGURE 7-38  
Dual-gate *n*-channel MOSFET symbols.

### SECTION 7-4 REVIEW

1. Name the two basic types of MOSFETs.
2. If the gate-to-source voltage in an *n*-channel depletion MOSFET is made more negative, does the drain current increase or decrease?
3. If the gate-to-source voltage in an *n*-channel E-MOSFET is made more positive, does the drain current increase or decrease?

### 7-5 MOSFET CHARACTERISTICS AND PARAMETERS

Much of the discussion concerning JFET characteristics and parameters applies equally to MOSFETs. In this section, MOSFET parameters are discussed.

After completing this section, you should be able to

- Define, discuss, and apply important MOSFET parameters
- Analyze a D-MOSFET transfer characteristic curve


- Use the equation for the D-MOSFET transfer characteristic to calculate  $I_D$
- Analyze an E-MOSFET transfer characteristic curve
- Use the equation for the E-MOSFET transfer characteristic to calculate  $I_D$
- Use a MOSFET data sheet
- Discuss handling precautions for MOS devices

### D-MOSFET Transfer Characteristic

As previously discussed, the D-MOSFET can operate with either positive or negative gate voltages. This is indicated on the general transfer characteristic curves in Figure 7-39 for both  $n$ -channel and  $p$ -channel MOSFETs. The point on the curves where  $V_{GS} = 0$  corresponds to  $I_{DSS}$ . The point where  $I_D = 0$  corresponds to  $V_{GS(off)}$ . As with the JFET,  $V_{GS(off)} = -V_P$ .

The square-law expression in Equation 7-1 for the JFET curve also applies to the D-MOSFET curve, as Example 7-13 demonstrates.

FIGURE 7-39  
D-MOSFET general transfer characteristic curves.

 

#### EXAMPLE 7-13

For a certain D-MOSFET,  $I_{DSS} = 10 \text{ mA}$  and  $V_{GS(off)} = -8 \text{ V}$ .

- (a) Is this an  $n$ -channel or a  $p$ -channel?
- (b) Calculate  $I_D$  at  $V_{GS} = -3 \text{ V}$ .
- (c) Calculate  $I_D$  at  $V_{GS} = +3 \text{ V}$ .

**Solution** (a) The device has a negative  $V_{GS(off)}$ ; therefore, it is an  $n$ -channel MOSFET.

$$(b) I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2 = (10 \text{ mA}) \left( 1 - \frac{-3 \text{ V}}{-8 \text{ V}} \right)^2 = 3.91 \text{ mA}$$


$$(c) I_D = (10 \text{ mA}) \left( 1 - \frac{+3 \text{ V}}{-8 \text{ V}} \right)^2 = 18.9 \text{ mA}$$

**Related Problem** For a certain D-MOSFET,  $I_{DSS} = 18 \text{ mA}$  and  $V_{GS(off)} = +10 \text{ V}$ .

- (a) Is this an  $n$ -channel or a  $p$ -channel?
- (b) Determine  $I_D$  at  $V_{GS} = +4 \text{ V}$ .
- (c) Determine  $I_D$  at  $V_{GS} = -4 \text{ V}$ .

### E-MOSFET Transfer Characteristic

The E-MOSFET uses only channel enhancement. Therefore, an *n*-channel device requires a positive gate-to-source voltage, and a *p*-channel device requires a negative gate-to-source voltage. Figure 7-40 shows the general transfer characteristic curves for both types of E-MOSFETs. As you can see, there is no drain current when  $V_{GS} = 0$ . Therefore, the E-MOSFET does not have a significant  $I_{DSS}$  parameter, as do the JFET and the D-MOSFET. Notice also that there is ideally no drain current until  $V_{GS}$  reaches a certain nonzero value called the *threshold voltage*,  $V_{GS(th)}$ .

 

**FIGURE 7-40**  
E-MOSFET general transfer characteristic curves.

The equation for the parabolic transfer characteristic curve of the E-MOSFET differs from that of the JFET and the D-MOSFET because the curve starts at  $V_{GS(th)}$  rather than  $V_{GS(off)}$  on the horizontal axis and never intersects the vertical axis. The equation for the E-MOSFET transfer characteristic curve is

$$I_D = K(V_{GS} - V_{GS(th)})^2$$

The constant  $K$  depends on the particular MOSFET and can be determined from the data sheet by taking the specified value of  $I_D$ , called  $I_{D(on)}$ , at the given value of  $V_{GS}$  and substituting the values into Equation 7-4. A typical E-MOSFET data sheet is given in Figure 7-41.

Equation 7-4

#### EXAMPLE 7-14

The data sheet in Figure 7-41 for a 2N7008 E-MOSFET gives  $I_{D(on)} = 500$  mA (minimum) at  $V_{GS} = 10$  V and  $V_{GS(th)} = 1$  V. Determine the drain current for  $V_{GS} = 5$  V.

**Solution** First, solve for  $K$  using Equation 7-4.

$$K = \frac{I_{D(on)}}{(V_{GS} - V_{GS(th)})^2} = \frac{500 \text{ mA}}{(10 \text{ V} - 1 \text{ V})^2} = \frac{500 \text{ mA}}{81 \text{ V}^2} = 6.17 \text{ mA/V}^2$$

Next, using the value of  $K$ , calculate  $I_D$  for  $V_{GS} = 5$  V.

$$I_D = K(V_{GS} - V_{GS(th)})^2 = (6.17 \text{ mA/V}^2)(5 \text{ V} - 1 \text{ V})^2 = 98.7 \text{ mA}$$

**Related Problem** The data sheet for an E-MOSFET gives  $I_{D(on)} = 100$  mA at  $V_{GS} = 8$  V and  $V_{GS(th)} = 4$  V. Find  $I_D$  when  $V_{GS} = 6$  V.

Maximum Ratings

Rating	Symbol	Value	Unit
Drain-Source voltage	$V_{DS}$	60	V dc
Drain-Gate voltage ( $R_{GS} = 1 \text{ M}\Omega$ )	$V_{DGR}$	60	V dc
Gate-Source voltage	$V_{GS}$	$\pm 40$	V dc
Drain current			mA dc
Continuous	$I_D$	150	
Pulsed	$I_{DM}$	1000	
Total power dissipation @ $T_A = 25^\circ\text{C}$	$P_D$	400	mW
Derate above $25^\circ\text{C}$		3.2	mW/ $^\circ\text{C}$
Operating and storage temperature range	$T_J, T_{stg}$	-55 to +150	$^\circ\text{C}$

Thermal Characteristics

Thermal resistance junction to ambient	$R_{\theta JA}$	312.5	$^\circ\text{C}/\text{W}$
Maximum lead temperature for soldering purposes, 1/16" from case for 10 seconds	$T_L$	300	$^\circ\text{C}$

Electrical Characteristics ( $T_C = 25^\circ\text{C}$  unless otherwise noted.)

Characteristic	Symbol	Min	Max	Unit
----------------	--------	-----	-----	------

OFF Characteristics

Drain-Source breakdown voltage ( $V_{GS} = 0, I_D = 100 \mu\text{A}$ )	$V_{(BR)DS}$	60	-	V dc
Zero gate voltage drain current ( $V_{DS} = 50 \text{ V}, V_{GS} = 0$ )	$I_{DSS}$	-	1.0	$\mu\text{A}$ dc
( $V_{DS} = 50 \text{ V}, V_{GS} = 0, T_J = 125^\circ\text{C}$ )		-	500	
Gate-Body leakage current, forward ( $V_{GSF} = 30 \text{ V dc}, V_{DS} = 0$ )	$I_{GSSF}$	-	-100	nA dc

ON Characteristics

Gate threshold voltage ( $V_{DS} = V_{GS}, I_D = 250 \mu\text{A}$ )	$V_{GS(th)}$	1.0	2.5	V dc
Static drain-source on-resistance ( $V_{GS} = 5.0 \text{ V dc}, I_D = 50 \text{ A dc}$ )	$r_{DS(on)}$	-	7.5	Ohm
( $V_{GS} = 10 \text{ V dc}, I_D = 500 \text{ mA dc}, T_C = 125^\circ\text{C}$ )		-	13.5	
Drain-Source on-voltage ( $V_{GS} = 5.0 \text{ V}, I_D = 50 \text{ mA}$ )	$V_{DS(on)}$	-	1.5	V dc
( $V_{GS} = 10 \text{ V}, I_D = 500 \text{ mA}$ )		-	3.75	
On-state drain current ( $V_{GS} = 10 \text{ V}, V_{DS} \geq 2.0 V_{D(on)}$ )	$I_{D(on)}$	500	-	mA
Forward transconductance ( $V_{DS} \geq 2.0 V_{D(on)}, I_D = 200 \text{ mA}$ )	$g_{fs}$	80	-	$\mu\text{mhos}$ or $\mu\text{S}$

Dynamic Characteristics


Input capacitance	$(V_{DS} = 25 \text{ V}, V_{GS} = 0, f = 1.0 \text{ MHz})$	$C_{iss}$	-	50	pF
Output capacitance		$C_{oss}$	-	25	
Reverse transfer capacitance		$C_{rss}$	-	5.0	

Switching Characteristics

Turn-On delay time	$(V_{DD} = 30 \text{ V}, I_D = 200 \text{ mA}, R_{gen} = 25 \text{ ohms}, R_L = 150 \text{ ohms})$	$t_{on}$	-	20	ns
Turn-Off delay time		$t_{off}$	-	20	

**2N7008**

Case 29-04, Style 22  
TO-92 (TO-226AA)

 

**TMOS FET Transistor**

*N* channel — Enhancement

FIGURE 7-41 Data sheet for the 2N7008 *n*-channel E-MOSFET (TMOSFET construction).

### Handling Precautions

All MOS devices are subject to damage from electrostatic discharge (ESD). Because the gate of a MOSFET is insulated from the channel, the input resistance is extremely high (ideally infinite). The gate leakage current,  $I_{GSS}$ , for a typical MOSFET is in the pA range, whereas the gate reverse current for a typical JFET is in the nA range. The input capacitance results from the insulated gate structure. Excess static charge can be accumulated because the input capacitance combines with the very high input resistance and can result in damage to the device. To avoid damage from ESD, certain precautions should be taken when handling MOSFETs:

1. MOS devices should be shipped and stored in conductive foam.
2. All instruments and metal benches used in assembly or test should be connected to earth ground (round or third prong of 110 V wall outlets).

3. The assembler's or handler's wrist should be connected to earth ground with a length of wire and a high-value series resistor.
4. Never remove a MOS device (or any other device, for that matter) from the circuit while the power is on.
5. Do not apply signals to a MOS device while the dc power supply is off.

### SECTION 7-5 REVIEW

1. What is the major difference in construction of the D-MOSFET and the E-MOSFET?
2. Name two parameters of an E-MOSFET that are not specified for D-MOSFETs?
3. What is ESD?

## 7-6 MOSFET BIASING

Three ways to bias a MOSFET are zero-bias, voltage-divider bias, and drain-feedback bias. Biasing is important in FET amplifiers, which you will study in the next chapter.

After completing this section, you should be able to


- Discuss and analyze MOSFET bias circuits
- Describe zero-bias of a D-MOSFET
- Analyze a zero-biased MOSFET circuit
- Describe voltage-divider bias of an E-MOSFET
- Describe drain-feedback bias of an E-MOSFET

### D-MOSFET Bias

Recall that D-MOSFETs can be operated with either positive or negative values of  $V_{GS}$ . A simple bias method is to set  $V_{GS} = 0$  so that an ac signal at the gate varies the gate-to-source voltage above and below this 0 V bias point. A MOSFET with zero bias is shown in Figure 7-42(a). Since  $V_{GS} = 0$ ,  $I_D = I_{DSS}$  as indicated. The drain-to-source voltage is expressed as follows:

$$V_{DS} = V_{DD} - I_{DSS}R_D$$

The purpose of  $R_G$  is to accommodate an ac signal input by isolating it from ground, as shown in Figure 7-42(b). Since there is no dc gate current,  $R_G$  does not affect the zero gate-to-source bias.

 

**FIGURE 7-42**  
A zero-biased D-MOSFET.